

Printed Page:-

Subject Code:- ACSBS0102

Roll. No:

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

NOIDA INSTITUTE OF ENGINEERING AND TECHNOLOGY, GREATER NOIDA

(An Autonomous Institute Affiliated to AKTU, Lucknow)

B.Tech

SEM: I - THEORY EXAMINATION (2022 - 2023)

Subject: Principles of Electrical Engineering

Time: 2 Hours

Max. Marks: 50

General Instructions:

IMP: Verify that you have received the question paper with the correct course, code, branch etc.

1. This Question paper comprises of **three Sections -A, B, & C.** It consists of Multiple Choice Questions (MCQ's) & Subjective type questions.
2. Maximum marks for each question are indicated on right -hand side of each question.
3. Illustrate your answers with neat sketches wherever necessary.
4. Assume suitable data if necessary.
5. Preferably, write the answers in sequential order.
6. No sheet should be left blank. Any written material after a blank sheet will not be evaluated/checked.

SECTION A

15

1. Attempt all parts:-

- | | | |
|-----|--|---|
| 1.a | Which unit is used to describe electric potential difference? (CO1) | 1 |
| | (a) Volts | |
| | (b) Ampere | |
| | (c) Joule | |
| | (d) Coulomb | |
| 1.b | In Superposition theorem, while considering a source, all other voltage sources are? (CO2) | 1 |
| | (a) Open circuited | |
| | (b) Short circuited | |
| | (c) Change its position | |
| | (d) Removed from the circuit | |
| 1.c | In a series L-C circuit at the resonant frequency the (CO3) | 1 |
| | (a) Current is maximum | |
| | (b) Current is minimum | |

- (c) Impedance is maximum
- (d) Voltage across C is minimum
- 1.d What happens to the capacitance when a dielectric material is inserted between the plates of a parallel plate capacitor? (CO4) 1
- (a) Capacitance decreases
- (b) Capacitance remains same
- (c) Capacitance increases
- (d) Depends upon the material of the dielectric
- 1.e Thermocouple generate output voltage according to _____(CO5) 1
- (a) Circuit parameters
- (b) Humidity
- (c) Temperature
- (d) Voltage

2. Attempt all parts:-


- 2.a Two resistor of 4Ω and 6Ω are connected in parallel. If the total current is 30 A. find the curent through each resistor. (CO1) 2
- 2.b Give two applications of the maximum power transfer theorem. (CO2) 2
- 2.c If $v = 200 \sin (377t - 30)$ V and $i = 8 \sin (377t - 30)$ A. What will be power factor? (CO3) 2
- 2.d What are the two components of no load current in a transformer?(CO4) 2
- 2.e What is earthing and its necessities in practical life . (CO5) 2

SECTION B

15

3. Answer any three of the following:-

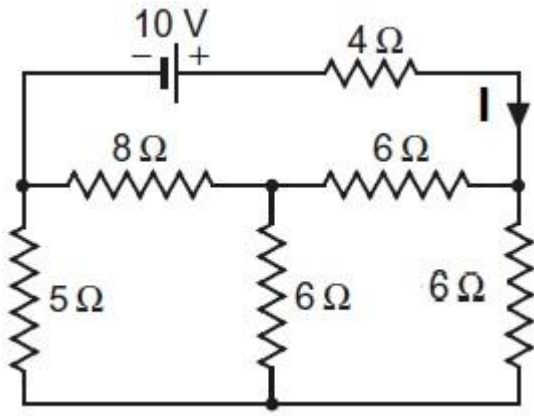- 3.a Three resistors are connected in series across a 12V battery. The first resistance has a value of 2Ω , second has a voltage drop of 4V and third has a power dissipation of 12W. Calculate the value of the circuit current. (CO1) 5
- 3.b Find current I in the network shown in Figure using star-delta transformation. (CO2) 5




- 3.c A current of 5A flows through a non-inductive resistance in series with a chok coil when supplied at 250 V, 50 Hz. If the voltage across the resistance is 125 V and across the coil is 200 V, calculate : (i) Impedance, reactance and resistance of the coil, (ii) The power absorbed by the coil, (iii) The total power supplied to the circuit. (CO3) 5
- 3.d Derive the emf equation of a single phase transformer also explain its working principle. (CO4) 5
- 3.e Explain the working principle of J type and K type thermocouple? Why reference junction compensation is important? (CO5) 5

SECTION C

20


4. Answer any one of the following:-

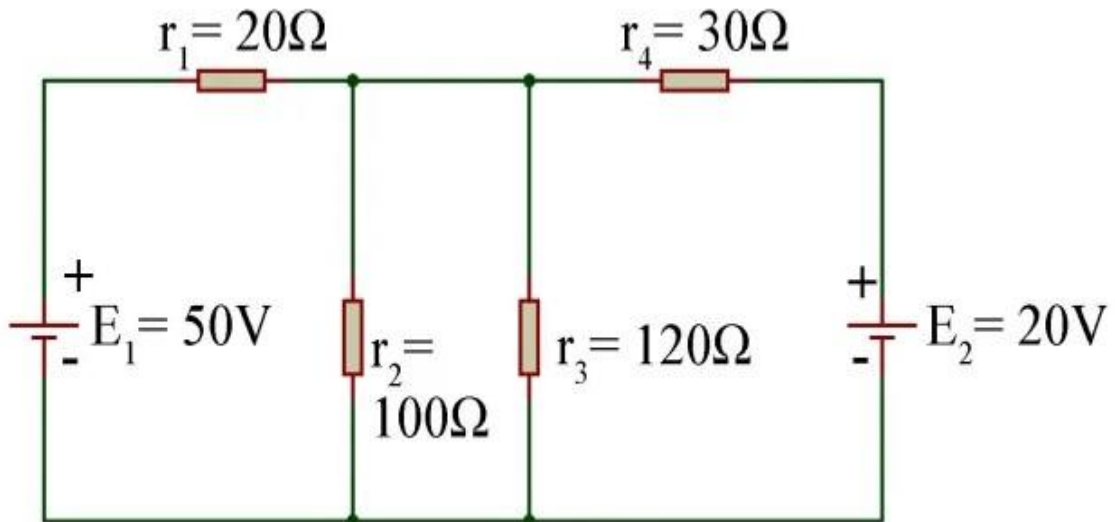- 4.a Using Nodal method, find the current through resistor r_2 . (CO1) 4



4.b Using mesh analysis , Calculate the currents I_1 and I_2 .(CO1)


4

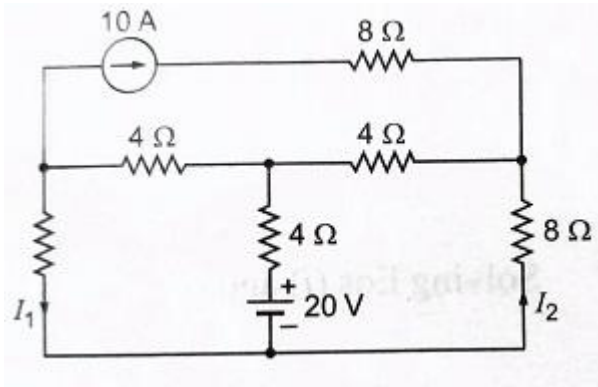

5. Answer any one of the following:-


5.a In the given circuit calculate current across 5Ω resistance by using superposition theorem. (CO2)

4

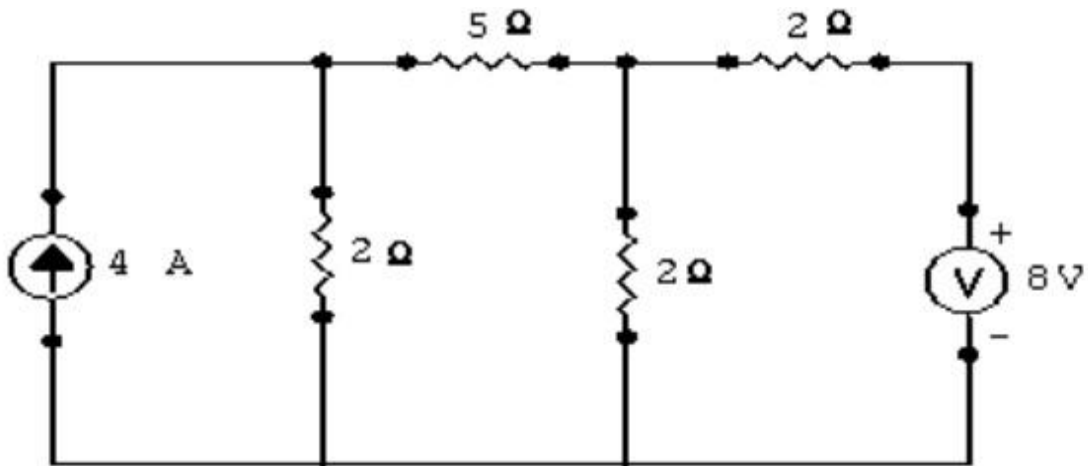

5.b Find the Thévenin equivalent circuit across terminals ab for the given network. (CO2)

4

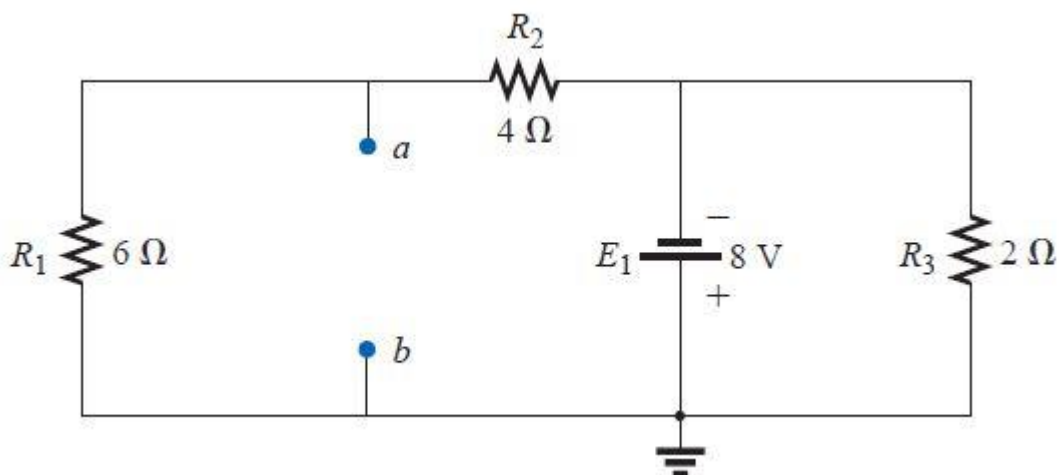

6. Answer any one of the following:-

6.a Define RMS and AVERAGE value of an alternating supply. Also derive the expressions of RMS and AVERAGE value for sinusoidal AC supply voltage. What is form factor and peak factor? (CO3)

4

- 6.b A three phase voltage source has a line voltage of 400 V and supplies star connected load having impedance $(8 + j6) \Omega$ per phase, calculate line current, power factor and total three phase power supplied to the load. (CO3) 4

7. Answer any one of the following:-

- 7.a Explain the principle of Electromechanical Energy Conversion and its applications. (CO4) 4
- 7.b In a 25 kVA, 2000/200 V transformer, the constant and variable losses are 350 W and 400 W respectively. Calculate the efficiency on unity power factor at (i) Full load, and (ii) Half load. (CO4) 4

8. Answer any one of the following:-

- 8.a What is piezo electric effect? Give name of four piezo electric materials. (CO5) 4
- 8.b Explain the working principle of battery. Also classify the types of batteries. (CO5) 4