

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

**NOIDA INSTITUTE OF ENGINEERING AND TECHNOLOGY, GREATER NOIDA**

(An Autonomous Institute Affiliated to AKTU, Lucknow)

**B.Tech**

**SEM: III - THEORY EXAMINATION (2023- 2024)**

**Subject: Digital System Design**

**Time: 3 Hours**

**Max. Marks: 100**

**General Instructions:**

**IMP:** Verify that you have received the question paper with the correct course, code, branch etc.

1. This Question paper comprises of **three Sections -A, B, & C**. It consists of Multiple Choice Questions (MCQ's) & Subjective type questions.
2. Maximum marks for each question are indicated on right -hand side of each question.
3. Illustrate your answers with neat sketches wherever necessary.
4. Assume suitable data if necessary.
5. Preferably, write the answers in sequential order.
6. No sheet should be left blank. Any written material after a blank sheet will not be evaluated/checked.

**SECTION-A**

20

1. Attempt all parts:-

1-a. Hamming code is capable of (CO1)

1

- (a) Only detect single-bit error
- (b) Only correct single-bit error
- (c) Detect and correct single bit error
- (d) Detect and correct multiple bit errors

1-b. The logical expression  $Y = \sum m(0, 3, 6, 7, 10, 12, 15)$  is equivalent to (CO1)

1

- (a)  $\pi M(0, 3, 6, 7, 10, 12, 15)$
- (b)  $\pi M(1, 2, 4, 5, 8, 9, 11, 13, 14)$
- (c)  $\sum m(1, 2, 4, 5, 8, 9, 11, 13, 14)$
- (d)  $\sum m(0, 2, 4, 6, 8, 10, 12, 14)$

1-c. How many data select lines are required for selecting eight inputs? (CO2)

1

- (a) 1
- (b) 2
- (c) 3
- (d) 4

1-d. The output of SUM is equal to output of (CO2)

1

- (a) OR gate
- (b) AND gate

- (c) X-OR gate
- (d) X-Nor gate
- 1-e. Why latches are called memory devices? (CO3) 1
- (a) It has capability to store 8 bits of data
- (b) It has internal memory of 4 bit
- (c) It can store one bit of data
- (d) It can store infinite amount of data
- 1-f. When both inputs of SR latches are high, the latch goes \_\_\_\_\_. (CO3) 1
- (a) Unstable
- (b) Stable
- (c) Indeterminate state
- (d) Bistable
- 1-g. Which of the following is the most widely employed logic family? (CO4) 1
- (a) Emitter-coupled logic
- (b) Transistor-transistor logic
- (c) PMOS logic
- (d) NMOS logic
- 1-h. Which of the following is the propagation delay of TTL circuits? (CO4) 1
- (a) 1 s
- (b) 1 ms
- (c) 1 ns
- (d) 1 ps
- 1-i. A typical SRAM cell is made up of .....Transistors. (CO5) 1
- (a) two
- (b) four
- (c) six
- (d) eight
- 1-j. For 5K memory, how many address lines are needed? (CO5) 1
- (a) 10
- (b) 13
- (c) 12
- (d) 9
2. Attempt all parts:-
- 2.a. Write the Demorgan's Theorem. (CO1) 2
- 2.b. Define Multiplexer. (CO2) 2
- 2.c. Write the advantages of sequential circuits? (CO3) 2
- 2.d. Define the terms : a) power dissipation b) Figure of merit. (CO4) 2



- 8-b. Describe the working of flash memory in detail with the help of a neat diagram. 10  
(CO5)

COP . JULY 2024