

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

**NOIDA INSTITUTE OF ENGINEERING AND TECHNOLOGY, GREATER NOIDA
(An Autonomous Institute Affiliated to AKTU, Lucknow)**

B.Tech

SEM:II CARRY OVER THEORY EXAMINATION- AUGUST 2023

Subject: Principles of Electronics

Time: 2 Hours

Max. Marks: 50

General Instructions:

IMP: Verify that you have received the question paper with the correct course, code, branch etc.

1. This Question paper comprises of **three Sections -A, B, & C.** It consists of Multiple Choice Questions (MCQ's) & Subjective type questions.
2. Maximum marks for each question are indicated on right -hand side of each question.
3. Illustrate your answers with neat sketches wherever necessary.
4. Assume suitable data if necessary.
5. Preferably, write the answers in sequential order.
6. No sheet should be left blank. Any written material after a blank sheet will not be evaluated/checked.

SECTION A

15

1. Attempt all parts:-

- 1-a. The energy level of electrons.....when they move away from the nucleus. (CO1) 1
- (a) Increases
 - (b) Decreases
 - (c) remains constant
 - (d) Becomes zero
- 1-b. The arrowhead in the diode symbol points the direction.....(CO2) 1
- (a) electron current
 - (b) conventional current
 - (c) reverse saturation current
 - (d) hole current
- 1-c. What is the left hand section of a junction transistor in CB called? (CO3) 1
- (a) base
 - (b) collector

- (c) emitter
- (d) depletion region

- 1-d. What is the value of current when the gate to source voltage is equal to the pinch off voltage? (CO4) 1
- (a) 1A
 - (b) 5A
 - (c) 100A
 - (d) 0
- 1-e. In order for an output to swing above and below a zero reference, the op-amp circuit requires.....(CO5) 1
- (a) a resistive feedback network
 - (b) zero offset
 - (c) a wide bandwidth
 - (d) a negative and positive supply

2. Attempt all parts:-

- 2.a. How p-type semiconductors are formed? (CO1) 2
- 2.b. Explain transition capacitance with reference to p-n junction diode. (CO2) 2
- 2.c. Why transistor is called a bipolar device? (CO3) 2
- 2.d. What is the major difference between a bipolar and unipolar device? (CO4) 2
- 2.e. Draw the circuit diagram of basic integrator using an OPAMP. (CO5) 2


SECTION B

15

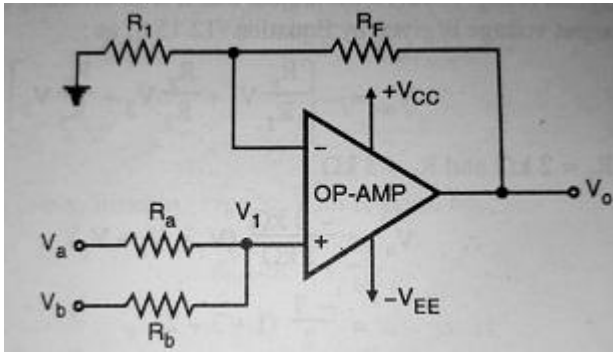3. Answer any three of the following:-

- 3-a. Write short notes on Fermi Level . Draw Fermi level in case of N type and P type semiconductor. (CO1) 5
- 3-b. Explain ideal and practical diode models. Draw the characteristics of an ideal diode. How does it differ from practical diode characteristics? (CO2) 5
- 3.c. What do you understand by "Transistor biasing" ? Mention the important points to be considered for the selection of operating point. The emitter current of a transistor is 10mA. If $\alpha = 0.99$ and $I_{CBO} = 10\mu A$. Calculate the value of I_C and I_B . (CO3) 5
- 3.d. Sketch the VI characteristics of JFET. Define pinch off voltage and mark it on the characteristics. Explain its importance. (CO4) 5
- 3.e. Derive the expression for output voltage of difference amplifier .If $V_a = +2V$ and $V_b = +4V$, $R_a = R_b = R_1 = 1k\Omega$ and $R_f = 3k\Omega$. Determine the voltage V_1 at 5

the non inverting terminal of OPAMP and the output voltage V_o . (CO5)



SECTION C

20

4. Answer any one of the following:-

- 4-a. With neat and clean energy band diagram classify conductors, semiconductors and Insulators. (CO1) 4
- 4-b. Differentiate between Intrinsic and Extrinsic semiconductor on the basis of carriers and conductivity. (CO1) 4

5. Answer any one of the following:-

- 5-a. A Diode operating at 300°K has V_F of 0.4V across it when the current through it is 10mA and 0.42V when the current is twice as large . What values of I_0 and η allow the diode to be modelled by the diode equation? (CO2) 4
- 5-b. Draw the circuit diagram of Bridge type full Wave Rectifier and explain its operation with output waveforms. (CO2) 4

6. Answer any one of the following:-

- 6-a. Draw output characteristics of CB configuration and explain different regions. (CO3) 4
- 6-b. Explain the different stability factors for BJT amplifier. What are the factors affecting the stability of Q Point? (CO3) 4

7. Answer any one of the following:-

- 7-a. What are the logic gates & types? Prove that the NAND and NOT gate are universal gates. (CO4) 4
- 7-b. What are the advantages of FET over BJT? How is an FET used as a voltage variable resistance? (CO4) 4

8. Answer any one of the following:-

- 8-a. What is a feedback amplifier? Briefly explain different types of feedback amplifiers. (CO5) 4
- 8-b. Design a summing amplifier to add three input voltages. The output of this circuit must be equal to 2 times the negative sum of the inputs. (CO5) 4