

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

NOIDA INSTITUTE OF ENGINEERING AND TECHNOLOGY, GREATER NOIDA
(An Autonomous Institute Affiliated to AKTU, Lucknow)

B.Tech

SEM: II - THEORY EXAMINATION (2023-2024)

Subject: Principles of Electronics

Time: 2 Hours

Max. Marks: 50

General Instructions:

IMP: Verify that you have received the question paper with the correct course, code, branch etc.

1. This Question paper comprises of **three Sections -A, B, & C.** It consists of Multiple Choice Questions (MCQ's) & Subjective type questions.
2. Maximum marks for each question are indicated on right -hand side of each question.
3. Illustrate your answers with neat sketches wherever necessary.
4. Assume suitable data if necessary.
5. Preferably, write the answers in sequential order.
6. No sheet should be left blank. Any written material after a blank sheet will not be evaluated/checked.

SECTION A

15

1. Attempt all parts:-

- | | | |
|------|---|---|
| 1-a. | Free electrons exist in..... (CO1) | 1 |
| | <ul style="list-style-type: none"> (a) Valance band (b) Coduction band (c) Free band (d) Second band | |
| 1-b. | Zener diode is invariably used with.....(CO2) | 1 |
| | <ul style="list-style-type: none"> (a) Forward biased (b) Reverse biased (c) Equilibrium (d) Schottky barrier | |
| 1-c. | What is the left hand section of a junction transistor in CB called? (CO3) | 1 |
| | <ul style="list-style-type: none"> (a) Base (b) Collector (c) Emitter | |

(d) Depletion region

- 1-d. What is the main advantage of FET which makes it more useful in industrial applications? (CO4) 1
- (a) Voltage controlled operation
 - (b) Less cost
 - (c) Small size
 - (d) Semiconductor device
- 1-e. In which configuration is an op-amp typically used for voltage amplification? (CO5) 1
- (a) Inverting amplifier
 - (b) Non-inverting amplifier
 - (c) Voltage follower
 - (d) both (a) and (b)

2. Attempt all parts:-

- 2.a. What are donor and acceptor impurities? (CO1) 2
- 2.b. Compare pn junction and zener diode.(CO2) 2
- 2.c. Define NPN and PNP transistor with their symbols. (CO3) 2
- 2.d. How FET worked as VVR? (CO4) 2
- 2.e. Define CMRR and Slew Rate in reference to op-amp. (CO5) 2

SECTION B

15

3. Answer any three of the following:-

- 3-a. Discuss the current flow mechanism in a p-n junction under no bias.(CO1) 5
- 3-b. Draw neat and clean diagram of transition capacitance and explain with their CV characteristics. (CO2) 5
- 3.c. Draw circuit diagrams of different configurations of BJT and define their current amplification factors. (CO3) 5
- 3.d. Sketch the VI characteristics of JFET. Define pinch off voltage and mark it on the characteristics. Explain its importance.(CO4) 5
- 3.e. Draw and explain integral circuit using an op-amp. Derive its output expression. (CO5) 5

SECTION C

20

4. Answer any one of the following:-

- 4-a. What do you understand by energy bands in semiconductors? (CO1) 4

4-b. Explain the following terms: (a) Potential Barrier (b) Knee Voltage (c) Forward biased (d) Reverse biased. (CO1) 4

5. Answer any one of the following:-

5-a. Give the comparison of Half wave rectifier and full wave rectifier. (CO2) 4

5-b. Discuss avalanche breakdown mechanism in p-n junction diode. (CO2) 4

6. Answer any one of the following:-

6-a. Explain the mechanism and principal of operation of BJT in brief. Also prove that $I_E = I_B + I_C$. (CO3) 4

6-b. Define and explain the reverse leakage current of CB configuration. (CO3) 4

7. Answer any one of the following:-

7-a. Define transconductance (g_m). Determine the transconductance (g_m) of JFET if there is a change in I_D of 0.6A with respect to change in V_{GS} of 0.2V. (CO4) 4

7-b. What is Full-Subtractor? Explain with the help of truth table and logic circuit diagram. (CO4) 4

8. Answer any one of the following:-

8-a. Define differential gain, common mode gain for differential amplifier and calculate the output voltage. (CO5) 4

8-b. In a feedback circuit, the input resistor $R_1 = 15K\Omega$, and feedback resistor $R_f = 90K\Omega$. Calculate the output voltage for 1V input for both inverting and non-inverting configurations. (CO5) 4