



Q.No.	Question Content	Question Image	Category	Sub Category	Marks	Options Randomization	Type	Difficulty
10	What is SRAM? Explain with the help of circuit diagram.		Attempt any 10 questions	10 x 3=30	3		Subjective	Smart
11	What is the function of full adder?		Attempt any 10 questions	10 x 3=30	3		Subjective	Brilliant
12	What is multiplexer and its types?		Attempt any 10 questions	10 x 3=30	3		Subjective	Brilliant
13	What is difference between average power and energy?		Attempt any 10 questions	10 x 3=30	3		Subjective	Brilliant
14	What is J K Flip Flop? Explain.		Attempt any 10 questions	10 x 3=30	3		Subjective	Brilliant
15	What does activity factor means? Explain.		Attempt any 10 questions	10 x 3=30	3		Subjective	Brilliant